

Class Report 2: 6.5.6 Reaction Timer

Samuel Hussey

1 Introduction

In this project, a reaction timer circuit was designed and implemented in which a user may initiate a test of their reflexes by pressing a button and waiting for an led to illuminate during a random interval between 2 and 15 seconds. During this time, an led onboard the Nexys4 will illuminate and the user must push a button as quickly as possible to record their time. The timer display will halt if the user takes longer than 1 second to react, but if the button is pressed before the led turns on the display will show '9999' and the test must be restarted. Source files can be found [here](#) and a video demonstration [here](#).

2 Implementation

The implementation of the circuit began with the design of 4 individual timer modules, each to control the count of a digit on the 7-segment display. This approach was chosen over a binary to binary-coded decimal converter for simplicity's sake. Each timer counts up to 9 at millisecond, centisecond, decisecond, and second speeds while driving the output to a time-multiplexed 7-segment display driver. A final timer was then used to coordinate the display with the 7-segment display output. A state machine is used to implement the rules of the test and coordinate the user interface buttons with the timers and display. A design sketch of the circuit is shown in figure 1.

3 Results

The simulated timing diagram is shown in figure 2. This figure demonstrates the 7-segment outputs changing in conjunction with the button input stimulus. The display shows the message 'HI' until btn[0] is pressed. This is followed by the display turning off while the simulated user waits for the led to illuminate. Pressing the 'clear button' returns the circuit to its original state.

4 Discussion

The use of 5 separate timers made for a crude implementation and proved difficult to coordinate during state transitions. In the future, a single timer counter and decimal converter would be a more elegant and simple approach. Issues were also encountered with random interval generation. Ultimately, the solution was to utilize a constantly running mod-m timer and check its value against a hard coded constant. Though not random, the impression of randomness is given depending on how the user interacts with the application.

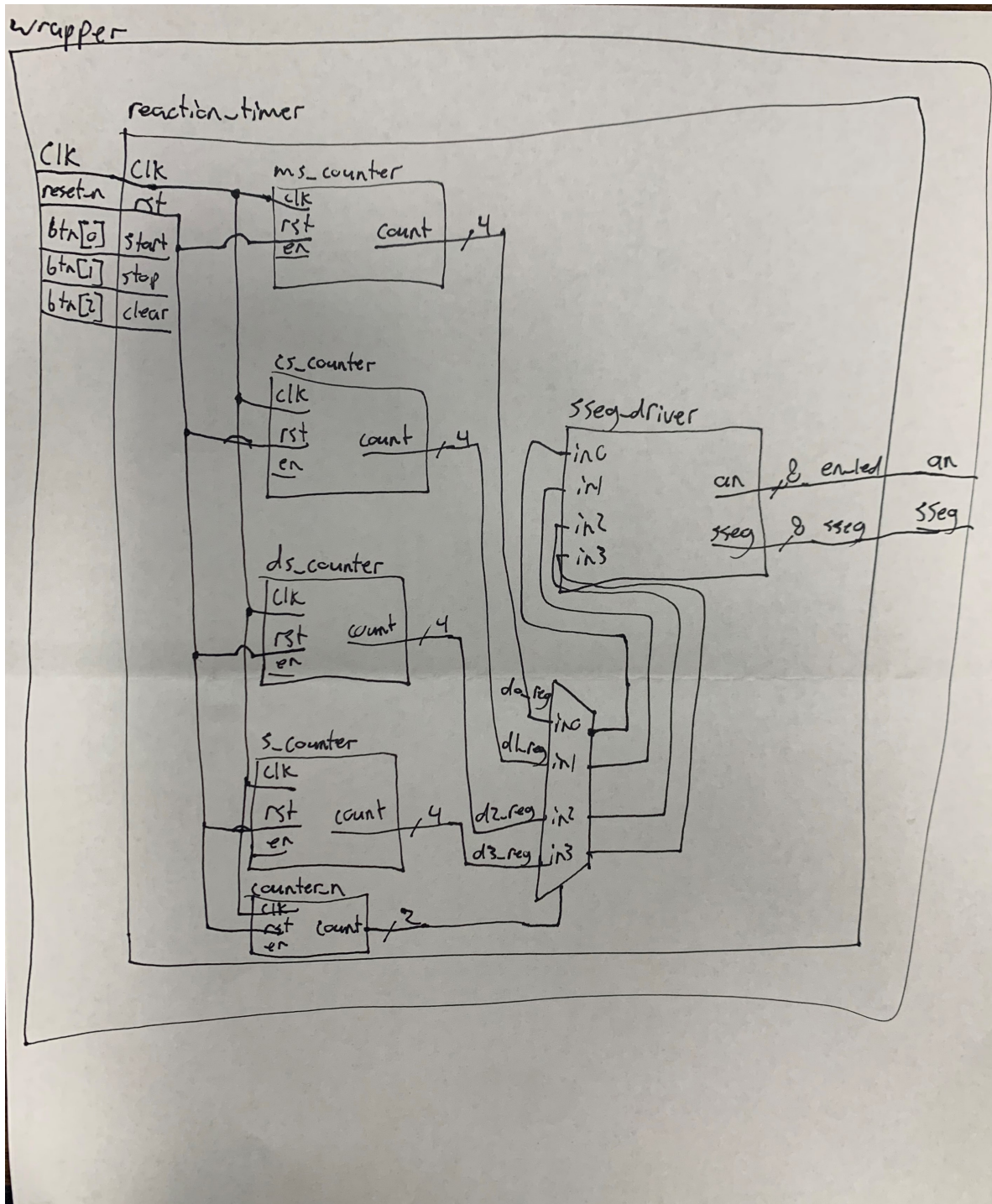


Figure 1: Design sketch of rotating square circuit.

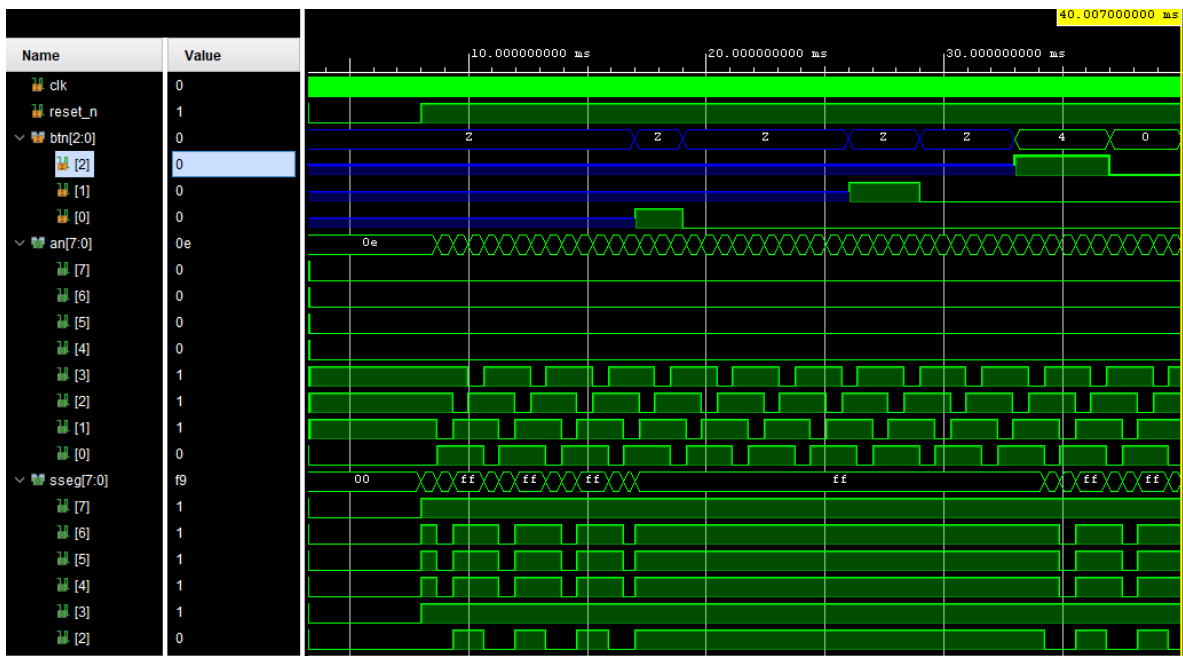


Figure 2: Timing diagram of testbench.